

I B. Tech II Semester Supplementary Examinations, March- 2022
BASIC ELECTRICAL AND ELECTRONICS ENGINEERING
 (ME, AME, Min E, Pet E, Food E, Pharm. E)


Time: 3 hours

Max. Marks: 70

Answer any five Questions one Question from Each Unit
All Questions Carry Equal Marks

Unit I

- 1 a) Derive an expression for the equivalent inductance when the inductances are connected in series. (7M)
- b) A resistance of 10 ohms is connected in series with a combination of two resistances arranged in parallel each of value 20 ohms. Determine the resistance R_3 which should be shunted across the parallel combination so that current drawn by the circuit is 1.5 A with applied voltage of 20 V. (7M)
- Or
- 2 a) State and explain Ohms law. (4M)
- b) Obtain the equivalent resistance across 'ad' for the following circuit: (10M)

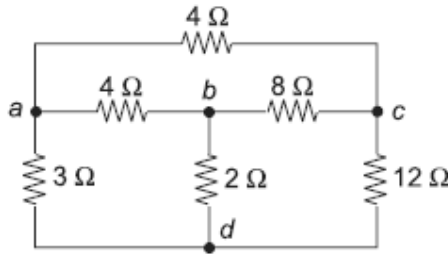**Unit II**

- 3 a) Derive the emf equation of a DC machine. (8M)
- b) A 6-pole 2 circuit wave connected armature has 250 conductors and runs at 1200 rpm. The electromotive force generated on open circuit is 600V. Determine the useful flux per pole. (6M)
- Or
- 4 a) Explain how the speed of a DC Shunt motor can be controlled and classify the methods. (7M)
- b) Swinburne test gave the following results on a de shunt motor: (7M)
 Supply voltage 500 V, no load current 5 A, Armature resistance 0.5 Ω and Field resistance 250 Ω . Determine the efficiency of the machine (i) as a generator delivering 100 A at 500 V (ii) as a motor having a line current of 100 A at 500 V Neglect temperature rise during operation. Assume stray losses at 1 % of output.

Unit III

- 5 a) Enumerate the various losses in a Single-phase transformer and how these can be minimized (7M)
- b) A single-phase transformer has 400 primary and 1000 secondary turns. The net cross-sectional area of core is 60 cm². If the primary winding be connected to 50 Hz supply at 520 V, calculate (i) the peak value of flux density in the core; (ii) the voltage induced in the secondary winding. (7M)



Or

- 6 a) Explain the difference between salient pole and cylindrical pole type of rotor used in alternators. (7M)
- b) A four-pole, three-phase, 50 Hz induction motor rotates at a speed of 1440 rpm. Calculate its slip percentage. Also calculate the frequency of the induced EMF in the rotor circuit. (7M)

Unit IV

- 7 a) What is a p – n junction and how it is formed and explain the significance of forward biased and reverse biased. (7M)
- b) Explain the operation of half wave rectifier circuit with corresponding circuit diagram and necessary input and output waveforms. (7M)

Or

- 8 a) Explain the operation of op – amp as a non - inverting amplifier. (7M)
- b) Explain how an op – amp can be used as a Differential amplifier (Subtractor). (7M)

Unit V

- 9 a) Explain the working of a n – p – n transistor with necessary diagrams. (7M)
- b) Illustrate the input and output characteristics of transistor in CE configuration. (7M)

Or

- 10 a) Explain how transistor is used as an amplifier with necessary diagram. (7M)
- b) Distinguish the significance between Active region, cut- off region and saturation region from the output characteristics of any configuration. (7M)

