

I B. Tech II Semester Regular/Supplementary Examinations, July/August - 2023
ELECTRICAL CIRCUIT ANALYSIS –I
(Only for Electrical and Electronics Engineering)


Time: 3 hours

Max. Marks: 70


Answer any five Questions one Question from Each Unit
All Questions Carry Equal Marks

UNIT-I

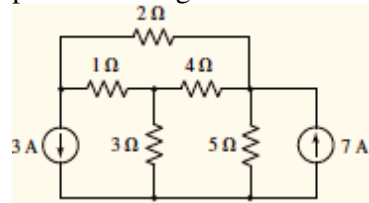
1. a) For the circuit shown, compute the voltage across each current source. [7M]



- b) Obtain the equivalent resistance at the terminals a-b [7M]

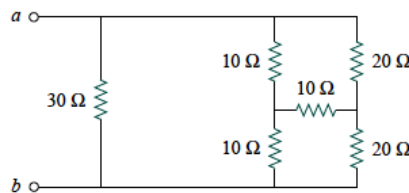**(OR)**

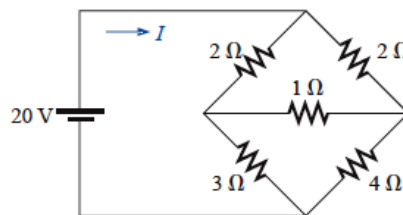2. a) Using a Δ -Y or Y- Δ conversion, find the current I in the network [7M]



- b) State and explain Kirchoff's Laws? [7M]

UNIT-II


3. a) Two identical coupled coils have an equivalent inductance of 80 mH when connected series aiding and 35 mH in series opposing. Find L_1 , L_2 , M and K . [7M]

- b) A closed magnetic circuit of cast steel contains a 6 cm long path of cross-sectional area 1 cm^2 and a 2 cm path of cross-sectional area 0.5 cm^2 . A coil of 200 turns is wound around the 6 cm length of the circuit and a current of 0.4A flows. Determine the flux density in the 2 cm path if the relative permeability of the cast steel is 750. [7M]

(OR)


4. a) Explain the analogy between electric and magnetic circuits? [7M]

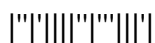- b) A magnetic circuit of cross-sectional area 0.4 cm^2 consists of one part 3 cm long, of material having relative permeability 1200, and a second part 2 cm long of material having relative permeability 750. With a 100-turn coil carrying 2A, find the value of flux existing in the circuit. [7M]



UNIT-III

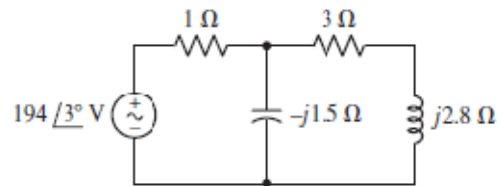
5. a) Calculate the average power absorbed by each passive element in the circuit shown, and verify that it equals the average power supplied by the source? [7M]



- b) A coil of inductance 159.2mH and resistance 20 Ω is connected in series with a 60Ω resistor to a 240V, 50 Hz supply. Determine (i) the impedance of the circuit, (ii) the current in the circuit, (iii) the circuit phase angle, (iv) the p.d. across the 60 Ω resistor and (v) the p.d. across the coil. (vi) Draw the circuit phasor diagram showing all voltages. [7M]

(OR)


6. a) The voltage of a circuit is $v = 200 \sin(\omega t + 30^\circ)$ and the current is $i = 50 \sin(\omega t + 60^\circ)$. Calculate i. The average power, reactive volt-amperes, and apparent power ii. Find the circuit elements if $\omega = 100\pi$ rad/sec. [7M]
- b) Determine the RMS value of the current waveform shown below? If this current waveform is passed through 2 Ω resistor find the average power absorbed by the resistor? [7M]

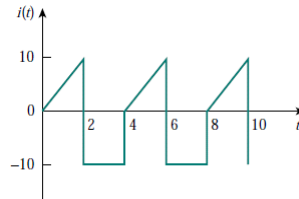**UNIT-IV**

7. a) A coil of resistance 25Ω and inductance 100mH is connected in series with a capacitance of 0.12 μF across a 200V, variable frequency supply. Calculate (i) the resonant frequency, (ii) the current at resonance and (iii) the factor by which the voltage across the reactance is greater than the supply voltage. [7M]
- b) A series RLC Circuit has a quality factor of 5 at 50 rad/s. The current flowing through the circuit at resonance is 10 A and the supply voltage is 100 V. Find the Circuit constants? [7M]


(OR)

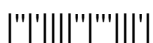8. a) A coil of 10 Ω resistance and 0.2 H inductance is connected in parallel with a variable capacitance across a 220 V, 50 Hz supply. Calculate (i) the capacitance of the capacitor for resonance (ii) the dynamic impedance of the circuit and the supply current. [7M]
- b) With a neat sketch explain series Locus diagram [7M]



UNIT-V

9. a) State and explain Milliman's theorem with an example? [7M]
 b) Apply the superposition principle to find i and power delivered to the $3\ \Omega$ resistor in the circuit shown below? [7M]

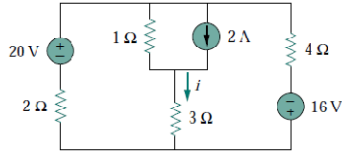**(OR)**

10. a) State and explain maximum power transfer theorem with an example for DC excitation? [7M]
 b) Obtain the Norton equivalent of the circuit in Fig. shown to the left of terminals a-b. Use the result to find current i . [7M]

