

**I B. Tech II Semester Supplementary Examinations, Jan/Feb-2024****NETWORK ANALYSIS**

(Common to ECE, EIE, ECT)


Time: 3 hours

Max. Marks: 70

*Answer any five Questions one Question from Each Unit*  
*All Questions Carry Equal Marks*

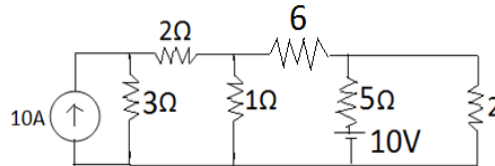**UNIT - I**


- 1 a) Determine the voltage across various elements of the circuit shown below by node analysis. [7M]



- b) A resistance R in series with a capacitor C is connected to 50 Hz, 240V, AC Supply. (i) Find the value of C so that R absorbs 300W at 100V. (b) Find the maximum charge and the maximum stored energy in C. [7M]

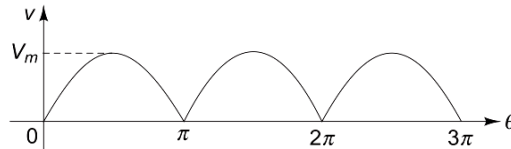**(OR)**

- 2 a) Find the average value and rms value of the waveform shown in below Figure. [7M]



- b) Define Tie Set and also discuss how to obtain Tie Set Matrix with a suitable example. [7M]

**UNIT-II**

- 3 a) Discuss the Transient Response of R-C series network with DC excitation. [7M]  
 b) Find the inverse Laplace Transform of  $X(s) = \frac{2s+4}{s^2+4s+3}$ . [7M]

**(OR)**


- 4 a) Explain about the Transient Response of R-L parallel network with DC excitation. [7M]  
 b) Describe and analyze the Transient Response of R-L-C parallel network with AC excitation. [7M]

**UNIT-III**

- 5 a) State the Dot Convention and also explain why it is necessary in magnetic circuits. [7M]  
 b) Two coils having 30 and 600 turns are wound side by side on a closed iron circuit of  $100 \text{ cm}^2$  cross section and mean length 150 cm. Find the self-inductance of the two coils and mutual inductance if relative permeability of iron is 2000. Assume no magnetic leakage. [7M]

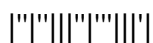**(OR)**

- 6 a) Briefly discuss about the steady state analysis of a series R-L circuit with AC Supply. [7M]  
 b) With an example explain coupled circuits. [7M]



**UNIT-IV**


- 7 a) Define Resonance and also discuss about circuit parameters versus frequency for series R L C circuit. [7M]
- b) A series R-L-C circuit consists of  $R=15\Omega$ ,  $L=0.02\Omega$ , &  $C=0.03\mu\text{F}$ . Calculate the frequency at resonance. If a 15V of frequency equal to the frequency of resonance is applied to the circuit, calculate the values of  $V_C$  and  $V_L$  across C and L respectively. Find the frequencies at which these voltages  $V_C$  and  $V_L$  are maximum. [7M]

**(OR)**

- 8 a) State and discuss about Maximum Power Transfer Theorem. [7M]
- b) Verify Tellegen's Theorem with a suitable example. [7M]

**UNIT-V**

- 9 a) Derive and discuss the relationships between Y and Z parameters. [7M]
- b) Find the ABCD parameters of the following network: [7M]

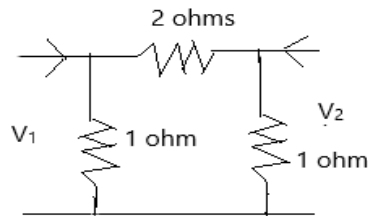**(OR)**

- 10 a) Discuss how to obtain H parameters with a suitable example. [7M]
- b) Write short notes on relationship between parameter sets. [7M]

\*\*\*\*\*

