

**I B. Tech II Semester Regular/Supplementary Examinations, July/August-2023****NETWORK ANALYSIS**


(Common to ECE, EIE, ECT)

Time: 3 hours


Max. Marks: 70

*Answer any five Questions one Question from Each Unit**All Questions Carry Equal Marks***UNIT - I**


- 1 a) What are the classifications of network elements? Discuss them. [5M]  
 b) Calculate the current in  $5\ \Omega$  resistor by using Kirchoff's laws as shown in below figure. [9M]

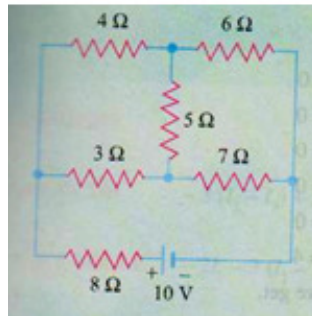**(OR)**


- 2 a) Define the following [7M]  
 RMS value, (ii) Average value, (iii) Form factor and (iv) peak factor  
 b) Construct the dual for the network shown in Figure. Also, explain the procedure used. [7M]

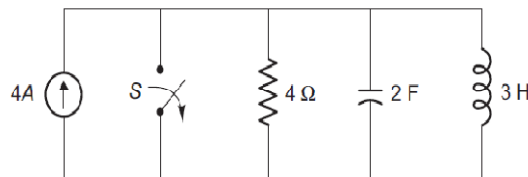**UNIT-II**

- 3 a) Describe the study of initial conditions of circuit parameters [5M]  
 b) Find the transient current  $i(t)$  for the network shown in figure. At  $t=0$ , the switch S is closed. Find the voltage across inductor and capacitor. [9M]

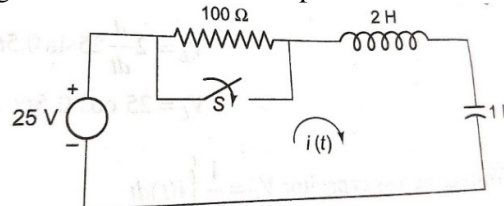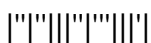
**(OR)**

- 4 a) Describe the Laplace Transform of signal waveforms with necessary diagrams and expressions. [6M]




- b) Find the current through the inductor for  $t > 0$  in figure.

[8M]

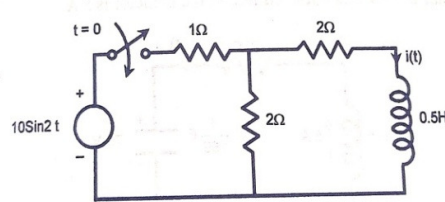**UNIT-III**

- 5 Find the mesh currents for the network shown in figure.

[14M]

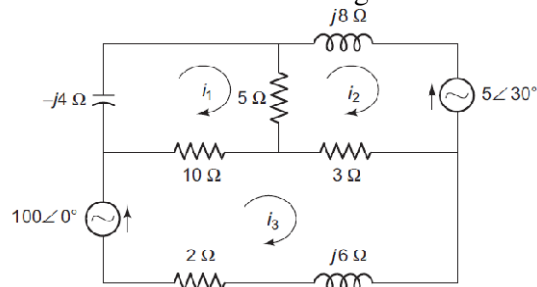**(OR)**



- 6 a) Derive the expression for coefficient of coupling of magnetic circuit. [7M]  
 b) For the series connection of two coupled coils, find the expression for mutual inductance. When the fluxes of the two coils assist each other, the net equivalent inductance is  $L_1$  and when the fluxes of the two coils oppose each other, the equivalent inductance is  $L_2$ . [7M]

**UNIT-IV**

- 7 a) Derive the expression for resonant frequency in terms of half power frequencies. [7M]  
 b) Following are parameters for a series  $RLC$  circuit:  $R = 50$  ohms,  $L = 0.5$  H and  $C = 30$   $\mu$ F. If a constant voltage of 230 V, at variable frequency is applied, find the frequency at which resonance occurs. Also find maximum voltages across  $L$  and  $C$ . [7M]

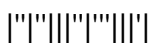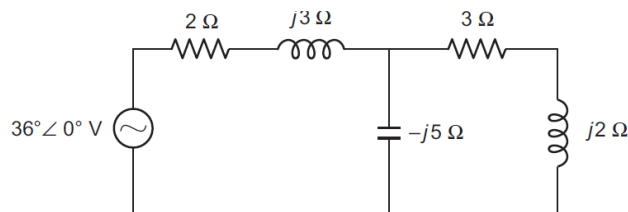
**(OR)**

- 8 a) State and explain the Substitution theorem. [6M]  
 b) For the circuit shown in Figure, verify the reciprocity theorem. [8M]




**UNIT-V**


- 9 a) Obtain the transmission parameters in terms of Z and Y-parameters. [6M]  
 b) Find the *ABCD* parameters of the circuit shown in Figure. [8M]

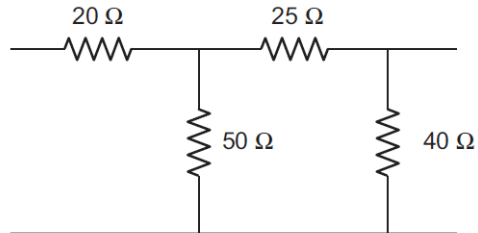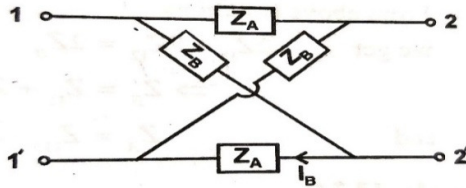**(OR)**

- 10 a) Obtain the conditions for reciprocity and symmetry for Z-parameters. [6M]  
 b) The network shown in figure is known as a lattice network. Find (i) Z-parameters of the lattice network and (ii) express  $Z_A$  and  $Z_B$  in terms of Z-parameters. [8M]



\*\*\*\*\*

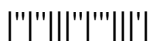

**I B. Tech II Semester Regular/Supplementary Examinations, July/August-2023****NETWORK ANALYSIS**

(Common to ECE, EIE, ECT)

Time: 3 hours


Max. Marks: 70

*Answer any five Questions one Question from Each Unit**All Questions Carry Equal Marks***UNIT - I**


- 1 a) Define the following [6M]  
 (i) Electric charge (ii) Current (iii) Electric energy (iv) Potential
- b) A Wheatstone bridge ABCD is arranged as follows:  $AB = 1 \Omega$ ,  $BC = 2 \Omega$ ,  $CD = 3 \Omega$ ;  $DA = 4 \Omega$ . A resistance of  $5 \Omega$  connected between B and D. A 20-volt battery of internal resistance  $1 \Omega$  is connected between A and C. Calculate i) The magnitude and direction of current in  $5 \Omega$  resistor and ii) the resistance between A and C. [8M]

**(OR)**



- 2 a) Explain the procedure for obtaining fundamental tie set matrix of a given network [6M]
- b) For the circuit shown in below figure, find the resistance between the terminals A and B. [8M]

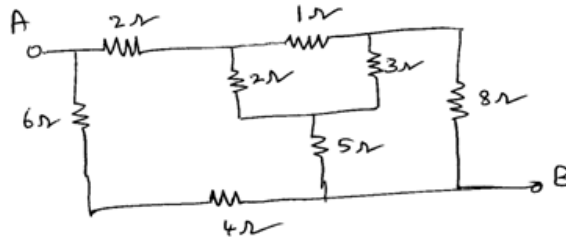**UNIT-II**

- 3 a) Explain the procedure evaluating initial conditions of circuit parameters [7M]
- b) For the circuit given in the figure, find the transient current and also determine the voltage drop across resistor and capacitor when switch S is closed at  $t=0$ . [7M]

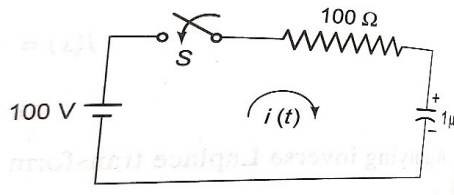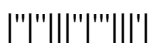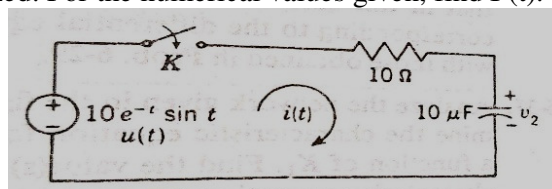**(OR)**

- 4 a) Explain the differences between first order and second order differential equations. [7M]
- b) In the network of the figure, the switch S is closed at  $t=0$  with the capacitor initially unenergized. For the numerical values given, find  $I(t)$ . [7M]



## UNIT-III

- 5 a) Explain the mesh analysis with suitable circuit diagram and derive its expressions [7M]  
 b) A voltage of  $(100 + j40)$  volts drives a current of  $(4 - j6)$  Amp through a series R-L-C Circuit. Determine the following [7M]  
 i) The complex expression for impedance  
 ii) Power consumed  
 iii) Power factor  
 iv) Draw the phasor diagram

(OR)


- 6 a) Explain the dot convention with suitable diagrams [7M]  
 b) An iron ring of mean length 150 cm with an air gap of 1mm has a winding of 600 turns and the relative permeability of iron is 600. When a current of 5 A flows in the winding, determine flux density. Neglect leakage and fringe ring. [7M]

## UNIT-IV

- 7 a) Derive the expression for Q factor and bandwidth of parallel RLC circuit at resonance [7M]  
 b) An impedance coil having resistance of 28ohms and inductance 28 mH is connected in parallel with variable capacitors. Determine value of C when the circuit undergoes resonance if a 100 V, 430 Hz source is applied. Find also the line current under resonance. [7M]



(OR)

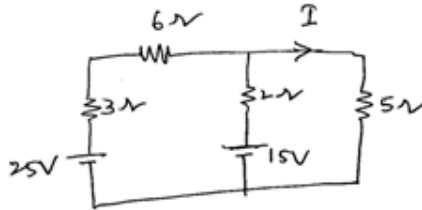- 8 a) State and explain the Milliman's theorem [6M]  
 b) Determine the current I in the network by using Thevenin's theorem as shown in below figure. [8M]



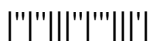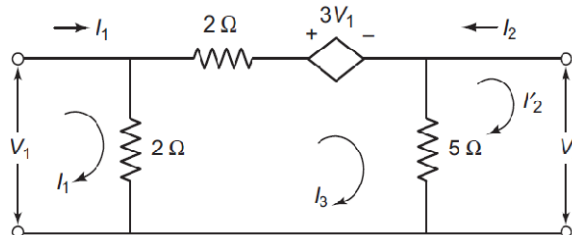
## UNIT-V

- 9 a) Obtain the relationships between Y-parameters in terms of ABCD parameters. [6M]  
 b) Find the Z-parameters of the circuit shown in Figure. [8M]



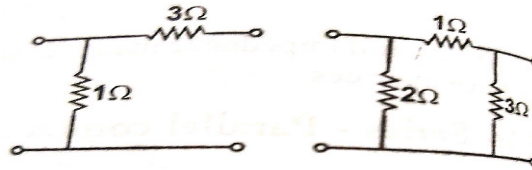**(OR)**

- 10 a) Obtain the conditions for reciprocity and symmetry for transmission-parameters. [7M]  
b) Connect in parallel the two circuits shown in figure and find Y-parameters. [7M]



\*\*\*\*\*

3 of 3



**I B. Tech II Semester Regular/Supplementary Examinations, July/August-2023****NETWORK ANALYSIS**

(Common to ECE, EIE, ECT)


Time: 3 hours

Max. Marks: 70


*Answer any five Questions one Question from Each Unit  
All Questions Carry Equal Marks*

**UNIT - I**


- 1 a) Explain Independent and dependent sources with their characteristics. [7M]  
 b) For the circuit as show in following figure, determine the value of the current  $I_2$  and source voltage  $V_s$  ( All resistance are in ohms). [7M]

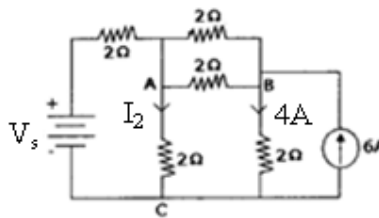**(OR)**


- 2 a) Definition the following [7M]  
 (i) Branch (ii) Node (iii) Tree (iv) Planar Graph  
 b) For the wave form as shown in below figure, calculate the RMS value and Average value: hence the value of form factor. [7M]

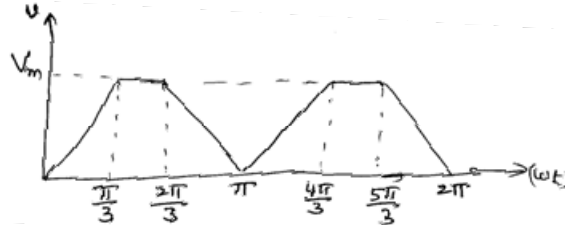**UNIT-II**


- 3 a) What are initial conditions? Why are they necessary? [6M]  
 b) Find the transient current  $i(t)$  for the network shown in figure. At  $t=0$ , the switch S is closed. Find the voltage across inductor and capacitor. [8M]

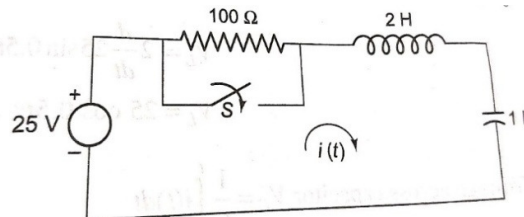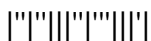**(OR)**

- 4 a) Distinguish between classical and Laplace transform methods of solution of a circuit. [6M]




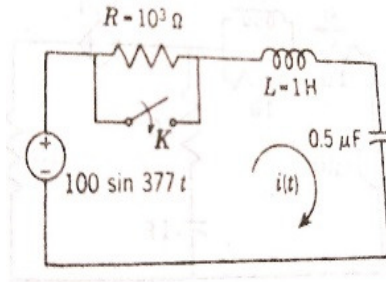- b) In the network shown in the accompanying figure, a steady state is reached with the switch S is open. AT  $t = 0$ , the switch is closed. For the element values given, determine the current,  $i(t)$  for  $t \geq 0$ . [8M]


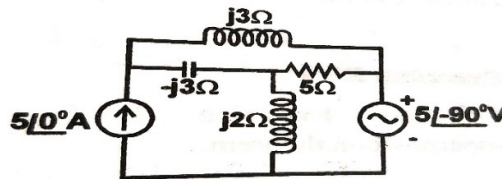
## UNIT-III

- 5 Determine all mesh currents for the circuit shown in figure using mesh analysis. [14M]





- 6 a) Compare between magnetic circuits and electrical circuits. [6M]  
 b) An iron ring of mean circumference 50 cm and a circular cross-sectional area of  $2 \text{ cm}^2$  has a saw cut 2 mm in length and is wound with 300 turns of wire. If a 1 mWb flux exists across the air gap, find the exciting current. Take leakage factor as 1.6 and  $\mu_r$  for iron as 500. [8M]

## UNIT-IV

- 7 a) Derive the resonance frequency of parallel circuit considering internal resistances of L only. [7M]  
 b) Calculate half-power frequencies of a resonant circuit where the resonant frequency is 255 kHz and the bandwidth is 150 kHz. [7M]

(OR)

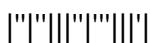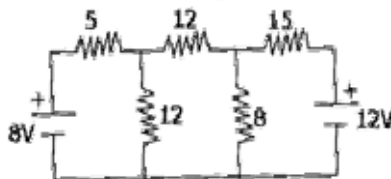
- 8 a) State and explain the Compensation theorem. [6M]  
 b) Using superposition theorem calculates the current in 8 ohms resistances shown in following figure (All resistance is in ohms). [8M]





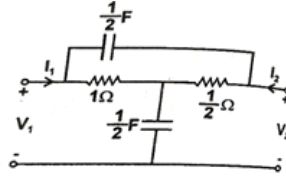
## UNIT-V

- 9 a) Obtain the relationships between Z-parameters in terms of h- parameters. [7M]  
 b) The network shown in figure is known as bridge T-network. Determine Y-parameters of the network. [7M]



(OR)

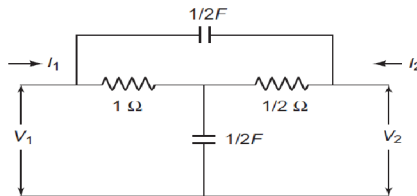- 10 a) Obtain the conditions for reciprocity and symmetry for h-parameters. [6M]  
 b) Find the ABCD parameters of the network shown in figure. [8M]



\*\*\*\*\*



**I B. Tech II Semester Regular/Supplementary Examinations, July/August-2023****NETWORK ANALYSIS**


(Common to ECE, EIE, ECT)

Time: 3 hours


Max. Marks: 70

*Answer any five Questions one Question from Each Unit**All Questions Carry Equal Marks***UNIT - I**


- 1 a) Definitions of terms associated with periodic functions [6M]  
 (i) Time period (ii) Angular velocity (iii) frequency
- b) Using nodal method, find the current through the 5 ohms resistor in the circuit show in the figure. [8M]

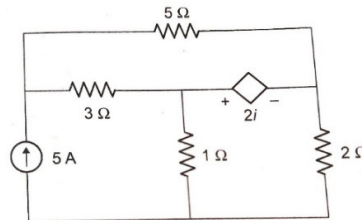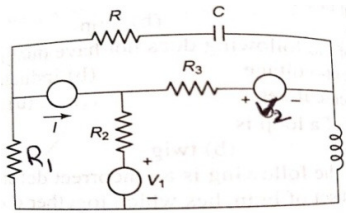**(OR)**



- 2 a) What is the Principal of Duality? Write the procedure for obtaining the dual of a given planer network shown in figure [7M]



- b) Determine the resistance between the points A and B of the network as shown in the figure? [7M]

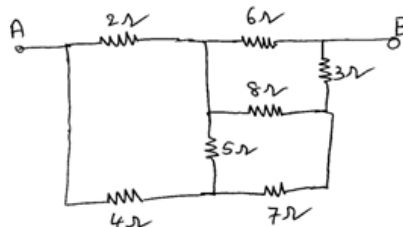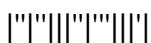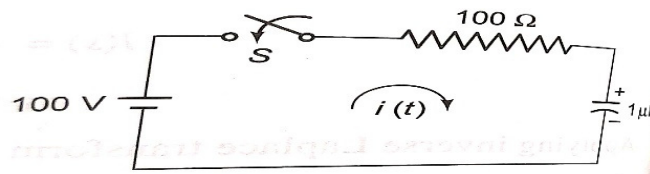
**UNIT-II**

- 3 a) Explain the evaluating initial conditions procedure. [7M]
- b) For the circuit given in the figure, find the transient current and also determine the voltage drop across resistor and capacitor when switch S is closed at  $t = 0$ . [7M]




(OR)

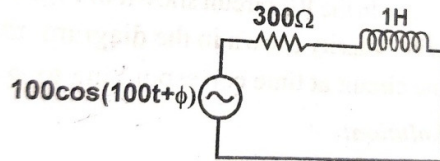- 4 a) Describe the Laplace Transform of signal waveforms with necessary diagrams and expressions. [7M]
- b) An RL series circuit with  $R = 300$  ohms and  $L = 1$  H has a sinusoidal voltage  $v = 100 \cos(100t + \phi)$  volts. If the switch is closed with  $\phi = 45^\circ$ , obtain the resulting current  $i(t)$ . [7M]



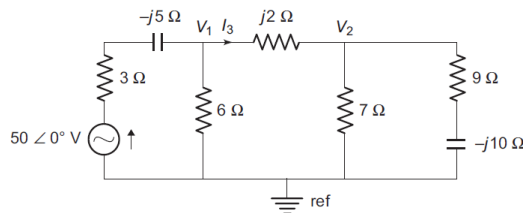
## UNIT-III

- 5 Determine the power supplied to the circuit shown in figure by a source  $V_1 = 50 \angle 0^\circ$  V. Also find the power dissipated by each resistor in the circuit using nodal method. [14M]




(OR)

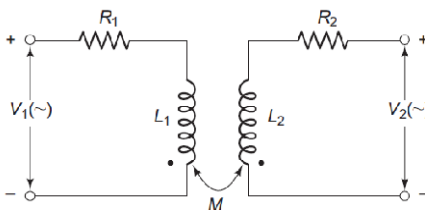- 6 a) Write down the dissimilarities of magnetic circuit and electric circuit. [6M]
- b) Find the value of mutual inductance for the circuit shown in Figure representing a coupled coil circuit where  $L_1 = 30$  mH,  $L_2 = 40$  mH, and coefficient of coupling,  $K = 0.6$ . Also write down the mesh equations in time domain. [8M]



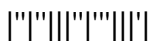
## UNIT-IV

- 7 a) Derive the resonance frequency of parallel circuit considering internal resistances of L and C. [7M]
- b) An impedance coil having resistance 15 ohms and inductance coil of 0.02 H is connected in series with 0.01  $\mu$ F capacitor. Calculate. [7M]
- $Q$  of coil
  - Resonant frequency of the circuit
  - Half-power frequencies




(OR)

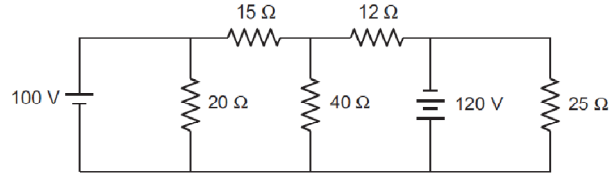- 8 a) State and explain the Tellegens theorem. [6M]  
 b) Using Millman's theorem to calculate voltage drop across the 40 ohms resistor of the network shown in figure. [8M]




UNIT-V

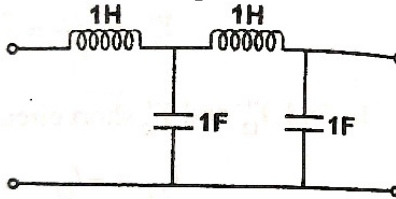- 9 a) Obtain the relationships between Y-parameters in terms of h- parameters [6M]  
 b) Find transmission parameters for the low pass filter network shown in figure. [8M]



(OR)

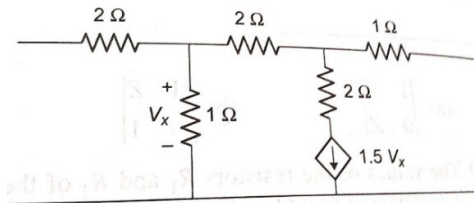- 10 a) Obtain the conditions for reciprocity and symmetry for Y-parameters. [6M]  
 b) Determine the Z-parameters for the network shown in the figure. [8M]



\*\*\*\*\*

