Code No: R201212 (R20) (SET - 1

I B. Tech II Semester Regular Examinations, September- 2021 OBJECT ORIENTED PROGRAMMING THROUGH JAVA

(Com. to ECE, EIE, ECT)

Time: 3 hours Max. Marks: 70

(7M)
(7M)
(=3.5)
m (7M)
(7M)
(7M)
etails (7M)
VA (7M)
(7M)
(7M)
(7M)
(7M)
(7M)
(7M)
(7M)
(7M)
(7M)
. (7M)
(7M)
ng (7M)
(7M) ol

1 of 1

1"['][[["]["][]]

Code No: R201220 (R20)

SET - 1

I B. Tech II Semester Regular Examinations, September- 2021 BASIC ELECTRICAL & ELECTRONICS ENGINEERING

(Comm. to CSE-CS&T, CSE-CS, CSE-IOT&CS incl BCT, CSE-CS&BS, CSE-IOT, Cyber Security)
Time: 3 hours

Max. Marks: 70


Answer any five Questions one Question from Each Unit All Questions Carry Equal Marks

UNIT-I

1 a) Explain the following terms:

(7M)

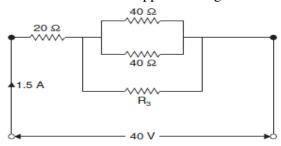- i) Potential Difference ii) Current
 - i) Current iii) passive elements iv) Active Elements
- v) Ideal Sources vi) Practical Sources vii) Dependent sources
- b) A resistance of 20 ohms is connected in series with a combination of two resistances arranged in parallel each of value 40 ohms. Determine the resistance R₃ which should be shunted across the parallel combination so that the total current drawn by the circuit is 1.5 A with applied voltage of 40 V.




Or

- 2 a) Derive an expression for the equivalent capacitance when the capacitances are connected in series. (7M)
 - (== E)

b) Determine the value of R such that $i_1 = 0.37A$

(7M)

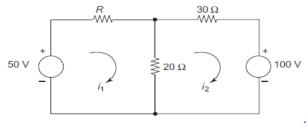


UNIT-II

3 a) State and explain Norton's theorem.

(7M)

b) Find the node voltages using Superposition theorem.

(7M)

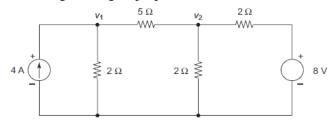

1 of 2

(7M)

(7M)

(7M)

Or

a) Distinguish between Active Power, Reactive Power and Apparent Power and also draw the Power triangle.
b) A coil takes 2.5 amps. When connected across 220-volt 50 Hz mains. The power (7M)

b) A coil takes 2.5 amps. When connected across 220-volt 50 Hz mains. The power consumed by the coil is found to be 400 watts. Find the inductance and the power factor of the coil.

UNIT-III

5 a) How are D.C. generators classified? Explain each one of them briefly and also give their applications. (7M)

b) A six-pole lap wound D.C. generator has 720 conductors, a flux of 40 m Wb per pole is driven at 400 r.p.m. Find the generated e.m.f.

Or

6 a) List and explain the various losses that are considered in a Single-phase transformer. (7M)

b) The no-load ratio required in a single-phase 50 Hz transformer is 6600/600 V. If the maximum value of flux in the core is to be about 0.08 Wb, find the number of turns in each winding.

UNIT-IV

7 a) Distinguish in detail between Salient pole type alternator and non-Salient pole (7M) alternator.

b) Derive an expression for voltage regulation of a three-phase synchronous generator. (7M)

Or


8 a) Explain the constructional of squirrel cage rotor type induction motor. (7M)

b) Draw and explain the Torque – Slip characteristic of a Three phase induction motor. (7M)

UNIT-V

9 a) Draw and explain the equivalent circuit of a Diode and its behavior under ideal and practical conditions. (7M)

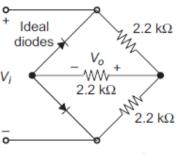b) For the following diode network, the sinusoidal input with $V_m = 170V$, determine V_o (dc)



Or

10 a) Draw and explain the Common collector configuration along with input and output characteristics. (7M)

b) Explain how an op- amp can be used as a Differentiator and Integrator.

2 of 2