

**II B. Tech I Semester Supplementary Examinations, July-2023**  
**ELECTRICAL CIRCUIT ANALYSIS - II**  
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions, each Question from each unit  
 All Questions carry **Equal** Marks

~~~~~  
 UNIT-I


- 1 a) Derive the relation between line and phase quantities in Delta connected system and also draw its phase diagrams. [7M]  
 b) A balanced, 3-phase star system consists of a load of 150 kW with a leading current of 100 A. [7M]  
 Find the circuit constants of the load per phase when a supply of 1100 V, 50 Hz is given to the system.

OR

- 2 a) Derive the necessary expressions for unbalanced delta connected load with neat diagrams. [7M]  
 b) A 400-V, 50-Hz, 3-phase supply of phase sequence *ABC* is applied to a delta-connected load consisting of 100 ohms between lines *A* and *B*, 318 mH inductance between lines *B* and *C*, and 31  $\mu$  F capacitance between lines *C* and *A*. Determine phase and line currents. [7M]


UNIT-II

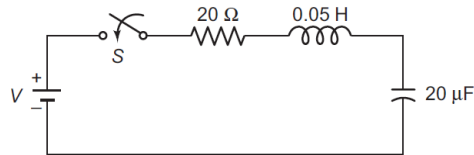- 3 a) Explain the initial conditions of R, L and C elements with necessary diagrams and expressions. [7M]  
 b) The circuit shown in Fig. consists of resistance, inductance and capacitance in series with a 200 V constant source when the switch is closed at  $t = 0$ . Find the current transient. Using differential equations. [7M]



OR

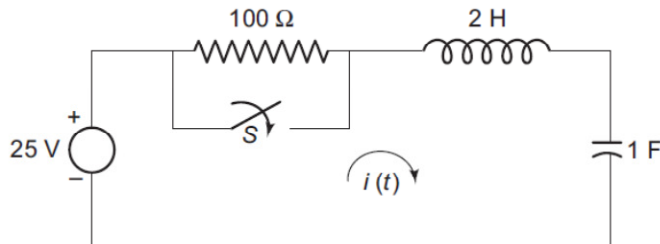- 4 Find the transition current  $i(t)$  for the network shown in Fig. At  $t = 0$ , the switch is closed. Find the voltage across inductor and capacitor and also find time taken at which  $V_L = V_C$ ? [14M]




Using Laplace transforms



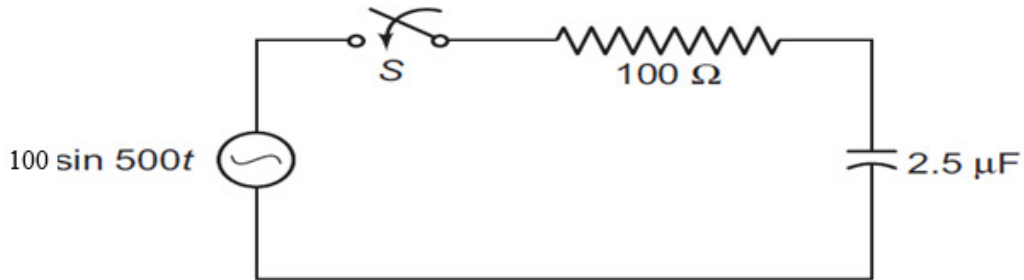
## UNIT-III

- 5 A series  $R$ - $C$  circuit with  $R = 100$  ohms and  $C = 2.5 \mu\text{F}$  as shown in figure has a sinusoidal voltage  $100 \sin 500t$ . Find the current assuming that there is no initial charge on the capacitor. Using differential equations. [14M]



OR

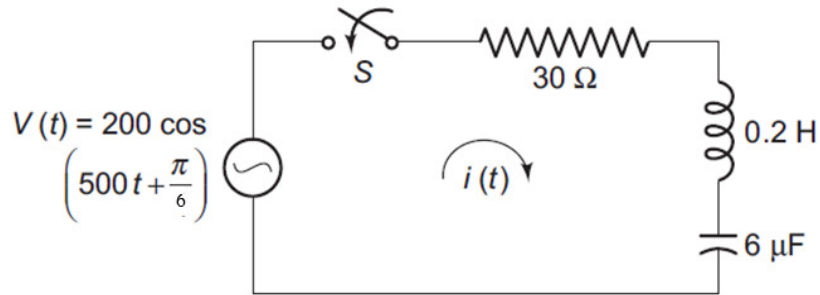
- 6 In the circuit shown in figure, determine the complete solution for the current, when the switch is closed at  $t = 0$ , applied voltage is  $v(t) = 200 \cos\left(500t + \frac{\pi}{6}\right)$ , resistance  $R = 30$  ohms, Inductance  $L = 0.2$  H and Capacitance  $C = 6 \mu\text{F}$ . [14M]



Using Laplace transforms
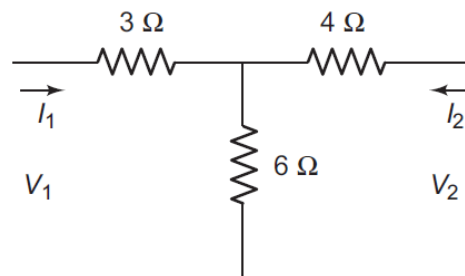
## UNIT-IV


- 7 a Obtain relationships between  $Y$ -parameters in terms of  $Z$ -parameters. [7M]  
b Determine the transmission parameters of the network shown in figure. [7M]



OR



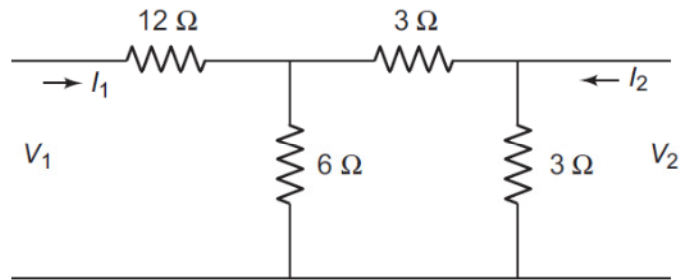- 8 a) Verify the condition for reciprocity and symmetry of Y-parameters. [7M]  
 b) Determine the h- parameters of the network shown in figure [7M]



UNIT-V

- 9 a) Explain the need of filters. [7M]  
 b) Design an  $m$ -derived low-pass filter having cut-off frequency of 1 kHz, resonant frequency 1500 Hz, and design impedance 750 ohms. [7M]

OR

- 10 a) Describe band elimination filter with necessary diagrams and expressions. [7M]  
 b) Draw the circuit diagram of series RL circuit that acts as a high pass filter. [7M]  
 (i) Write an expression for the circuit transfer function and (ii) find the value of R and L that will yield a high pass filter with a cutoff frequency of 10 kHz.

