

II B. Tech I Semester Regular Examinations, Feb/March - 2022
ELECTRONIC DEVICES AND CIRCUITS
 (Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unit
 All Questions carry **Equal** Marks

~~~~~

- |    |                                                                                                                                        |      |
|----|----------------------------------------------------------------------------------------------------------------------------------------|------|
| 1  | a) Explain about formation of PN Junction and how the diode acts as switch.                                                            | [7M] |
|    | b) Derive the expression for $E_G$ in case of intrinsic semiconductor.                                                                 | [7M] |
|    | Or                                                                                                                                     |      |
| 2  | a) Explain PN diode characteristics in forward bias and reverse bias regions.                                                          | [7M] |
|    | b) What is diffusion capacitance of a semiconductor diode? Explain how it arises.                                                      | [7M] |
| 3  | a) Explain V-I characteristics of a Tunnel diode with the help of its Fermi level diagram.                                             | [7M] |
|    | b) Explain construction and operation of a Half Wave rectifier and Find the PIV, RMS voltage ripple efficiency of Half Wave Rectifier. | [7M] |
|    | Or                                                                                                                                     |      |
| 4  | a) Explain about Varactor diode with characteristics.                                                                                  | [7M] |
|    | b) Derive the ripple factor and efficiency for full wave rectifier.                                                                    | [7M] |
| 5  | a) Explain with a neat sketch about various current components of a transistor?                                                        | [7M] |
|    | b) Explain about DC load line and AC load line? Explain the criteria for fixing operating point.                                       | [7M] |
|    | Or                                                                                                                                     |      |
| 6  | a) With the help of neat diagram, explain about operation of an N- channel JFET?                                                       | [7M] |
|    | b) Compare MOSFET with JFET.                                                                                                           | [7M] |
| 7  | a) Explain the input and output characteristics of a transistor in CB configuration.                                                   | [7M] |
|    | b) Why self-bias technique is so popular? And derive an expression for its stability factor.                                           | [7M] |
|    | Or                                                                                                                                     |      |
| 8  | a) With neat circuit diagram, explain the Voltage Divider Biasing.                                                                     | [7M] |
|    | b) Write a short note on Stabilization against variations in $V_{BE}$ and $\beta$ .                                                    | [7M] |
| 9  | a) Explain how h-parameters are determined from transistor characteristics.                                                            | [7M] |
|    | b) Explain the JFET Small signal Model.                                                                                                | [7M] |
|    | Or                                                                                                                                     |      |
| 10 | a) Explain the hybrid small signal model for common collector configuration.                                                           | [7M] |
|    | b) Explain the FET Common Drain Amplifier.                                                                                             | [7M] |