

II B. Tech I Semester Regular/Supplementary Examinations, December-2023
ELECTRONIC DEVICES AND CIRCUITS
 (Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unit
 All Questions carry **Equal** Marks

UNIT-I

- 1 a) Differentiate diffusion current and drift current. [7M]
 b) A Ge diode has a saturation current of $10\mu\text{A}$ at 300°K . Determine the saturation current at 400°K . [7M]

OR

- 2 a) Define the following: [8M]
 i. forward static and dynamic resistances of diode.
 ii. diffusion capacitance
 iii. transition capacitance.
 b) Show the position of Fermi level in N type and P type semiconductors. [6M]

UNIT-II

- 3 a) Explain the construction and operation of UJT. [7M]
 b) Explain how zener diode is used as a voltage regulator. [7M]

OR

- 4 a) A 230V, 60Hz voltage is applied to the primary of a 5:1 step down, center tapped transformer used in a full wave rectifier having a load of 900Ω . If the diode resistance and the secondary coil resistance together has a resistance of 100Ω , determine i) dc voltage across the load ii) dc current flowing through the load iii) dc power delivered to the load iv) PIV across each diode [10M]
 b) Give the advantages of LED. [4M]

UNIT-III

- 5 a) Describe early effect with relevant expressions and diagram. [7M]
 b) Mention the advantages and applications of JFET. [7M]

OR

- 6 a) With neat sketches and necessary waveforms, explain the input and output characteristics of a BJT in CE configuration. Also derive expression for output current. [9M]
 b) Identify and formulate the differences between BJT and FET. [5M]



UNIT-IV

- 7 a) Explain how self biasing can be done in a BJT with relevant sketches and waveforms. [7M]
b) Design a self bias circuit using silicon transistor to achieve a stability factor of 10, with the following specifications: $V_{CC} = 16V$, $V_{BE} = 0.7V$, $V_{CEQ} = 8V$, $I_{CQ} = 4 \text{ mA}$ & $\beta = 50$. [7M]

OR

- 8 a) Justify statement "Potential divider bias is the most commonly used biasing method" for BJT circuits. Explain how bias compensation can be done in such biasing through diodes. [7M]
b) Explain how I_{CO} variations are compensated with the help of diode and thermistor in transistor biasing circuits? [7M]

UNIT-V

- 9 a) Define all the four hybrid parameters of a BJT in CE configuration. Draw the circuit and its equivalent circuit. [6M]
b) A CE amplifier is driven by a voltage source of internal resistance $R_s = 800\Omega$ and the load impedance of $R_L = 1000\Omega$. The h-parameters are $h_{ie} = 1k$, $h_{fe} = 50$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Calculate current gain, voltage gain, input impedance and output impedance using exact analysis and approximate analysis. [8M]

OR

- 10 a) What is Two port network? [4M]
b) Derive input impedance, output impedance and voltage gain of JFET Common Drain amplifier with neat diagram. [10M]



II B. Tech I Semester Regular/Supplementary Examinations, December-2023
ELECTRONIC DEVICES AND CIRCUITS
(Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unit
All Questions carry **Equal** Marks

~~~~~

UNIT-I

- 1 a) Draw the energy band diagram of a semiconductor. Explain. [7M]  
b) Analyze the V-I characteristics of PN diode. [7M]

OR

- 2 a) Define the following: [6M]  
i. forward and reverse recovery time of a diode.  
ii. knee voltage and breakdown voltage  
b) State and derive the mathematical equation which relates voltage applied across the PN junction diode and current flowing through it and list the PN diode parameters. [8M]

UNIT-II

- 3 a) Draw the circuit of full-wave rectifier with capacitor filter. Explain its operation with necessary equations. [7M]  
b) Over what range of input voltage will the Zener in a voltage regulator in circuit maintain 30V across 2000  $\Omega$  load, assuming that series resistance  $R = 200\Omega$  and zener current rating is 25mA. [7M]

OR

- 4 a) Explain the V-I characteristics and application of SCR and explain its two transistor model. [8M]  
b) Compare HWR with FWR. [6M]

UNIT-III

- 5 a) Derive an expression for pinch off voltage in FET. [7M]  
b) Derive the relation between  $\alpha$  and  $\beta$  of a transistor. [7M]

OR

- 6 a) Describe the input and output characteristics of a transistor in CB configuration. [7M]  
b) Explain the mechanism of amplification in a transistor. [7M]

UNIT-IV

- 7 a) Draw a fixed bias circuit and explain its operation. Calculate the Stability factor. [7M]  
b) Sketch the basic circuit of a voltage amplifier and explain its action using load line analysis. [7M]

OR



- 8 a) Design a self bias circuit for the following specifications:  $V_{CC} = 12V$ ;  $V_{CE} = 2V$ ;  $I_C = 4mA$ ;  $h_{fe} = 80$ . Assume any other design parameters required. Draw the designed circuit. [7M]
- b) List out biasing techniques applied to the transistor? Mention their advantages and disadvantages. [7M]

## UNIT-V

- 9 a) Why hybrid model is used for the analysis of BJT amplifier at low frequencies? Explain. [4M]
- b) Determine Voltage Gain, Current Gain, Input resistance and Output resistance for a CE amplifier using NPN transistor with  $h_{ie} = 1200\Omega$ ,  $h_{re} = 0$ ,  $h_{fe} = 36$  and  $h_{oe} = 2 \times 10^{-6}$  mhos,  $R_L = 2.5k\Omega$  and  $R_S = 500\Omega$  (neglect the effect of biasing circuit) [10M]

## OR

- 10 a) What is the significance of exact and approximate analysis? [5M]
- b) Obtain the expression for current gain, voltage gain, input impedance and output impedance for Common Emitter Amplifier with Emitter Resistor. [9M]



**II B. Tech I Semester Regular/Supplementary Examinations, December-2023**  
**ELECTRONIC DEVICES AND CIRCUITS**  
(Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unit  
All Questions carry **Equal** Marks

~~~~~

UNIT-I

- 1 a) Examine the energy band structure of PN junction diode. [7M]
b) Explain about the effect of temperature on diode characteristics. [7M]

OR

- 2 a) Define Hall effect? Give some application of Hall Effect. [7M]
b) A silicon diode has a saturation current of $7.5\mu\text{A}$ at room temperature 300K. Calculate the saturation current at 400K. [7M]

UNIT-II

- 3 a) With neat diagram explain about varactor diode. [7M]
b) Draw the circuit diagram and explain the working of full wave rectifier and derive the expression for ripple factor, voltage, PIV Transformer Utilization Factor. [7M]

OR

- 4 a) Explain the operation of tunnel diode and draw its equivalent circuit. [7M]
b) Compare various filter circuits in terms of ripple factors. [7M]

UNIT-III

- 5 a) Explain input and output characteristics of a transistor in CC configuration. [7M]
b) List the classification of FET family and explain each component in detail. [7M]

OR

- 6 a) Compare among CC, CB, CE configurations of a transistor amplifier in terms of current gain, voltage gain, input impedance, output impedance and few applications. [7M]
b) Derive an expression for drain current of FET in pinch off region with necessary diagram. [7M]

UNIT-IV

- 7 a) An NPN Silicon transistor with $\beta=50$ is used in a common emitter circuit with $V_{CC}=10\text{V}$, $R_C=2\text{K}$. The bias is obtained by connecting a 100K resistance from collector to base. Find i) Q-Point ii) Stability factor, S [8M]
b) Write about Thermal Stability. [6M]

OR



- 8 a) Explain the basic requirements of transistor biasing. Verify these requirements in Emitter feedback bias circuit. [7M]
b) Design a collector to base bias circuit using silicon transistor to achieve a stability factor of 20, with the following specifications: $V_{CC} = 16V$, $V_{BE} = 0.7V$, $V_{CEQ} = 8V$, $I_{CQ} = 4 \text{ mA}$ & $\beta = 50$ [7M]

UNIT-V

- 9 a) The h parameters for the transistor are $h_{ie} = 1.1k\Omega$, $h_{fe} = 99$, $h_{re} = 2.5 \times 10^{-4}$ and $h_{oe} = 25 \mu A/V$. Find the h parameters for common base and common collector configurations [7M]
b) Compare the three configurations of JFET amplifiers. [7M]

OR

- 10 a) Determine the parameters A_i , R_i , A_v and R_o of Emitter Follower using simplified hybrid model analysis. [7M]
b) Write the expressions for mid-frequency gain of a FET Common Source Amplifier. [7M]



II B. Tech I Semester Regular/Supplementary Examinations, December-2023
ELECTRONIC DEVICES AND CIRCUITS
(Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unit
All Questions carry **Equal** Marks

~~~~~

UNIT-I

- 1 a) Derive the expression for PN junction diode forward and reverse currents with suitable diagram and necessary explanation [7M]  
b) Discuss about the following: [7M]  
i. Law of junction  
ii. Fermi Dirac function

OR

- 2 a) State and Prove Continuity equation. [7M]  
b) Determine the current in a PN Junction. Consider a PN junction at  $T = 300$  K in which  $I_s = 10^{-14}$  A and  $n = 1$ . Find the diode current for  $V_D = +0.70$  V and  $V_D = -0.70$  V. [7M]

UNIT-II

- 3 a) Explain the equivalent circuit, V-I characteristics of UJT. [7M]  
b) Explain the operation of a Half wave rectifier and its various parameters. [7M]

OR

- 4 a) Explain the operation of varactor diode. [6M]  
b) A full wave rectifier circuit uses two silicon diodes with a forward resistance of  $20\Omega$  each. A DC voltmeter connected across the load of  $1K\Omega$  reads 55.4 volts. Calculate i)  $I_{rms}$  ii) Average voltage across each diode iii) ripple factor iv) Transformer secondary voltage rating. [8M]

UNIT-III

- 5 a) Explain in detail about the Ebers Moll model. [7M]  
b) Compare the difference between JFET & MOSFET [7M]

OR

- 6 a) With neat diagram explain the operation of MOSFET in Depletion mode and derive its current equations [7M]  
b) Establish a relation between the three JFET parameters,  $\mu$ ,  $r_d$  and  $g_m$ . [7M]

UNIT-IV

- 7 a) Mention the need for transistor biasing? Explain. [7M]  
b) What is thermal runaway in transistors? Obtain the condition for thermal stability in transistors. [7M]

OR



- 8 a) Discuss about the following: [6M]  
i. DC load line ii. AC loadline  
b) Discuss about Stabilization against variations in  $V_{BE}$ ,  $I_C$ , and  $\beta$ . [8M]

## UNIT-V

- 9 a) Draw the hybrid model for CE transistor and derive the parameters. [7M]  
b) With the help of a neat schematic, explain the functioning of a common source amplifier. [7M]

## OR

- 10 a) Obtain the expressions for current gain, voltage gain, input impedance and output impedance of CB amplifier using simplified hybrid model. [8M]  
b) Compare the CE, CB and CC transistor amplifier parameters. [6M]

