

**II B. Tech I Semester Supplementary Examinations, July - 2022**  
**ELECTRONIC DEVICES AND CIRCUITS**  
(Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unit  
All Questions carry **Equal** Marks  
~~~~~

- 1 a) Explain about Hall effect. Derive an expression for Hall voltage. What are the applications of Hall effect? [9M]  
b) Explain in detail about the extrinsic and intrinsic semiconductors. [5M]  
Or
- 2 a) Derive an expression for total current in a semiconductor. [7M]  
b) Draw the Energy band diagram of PN diode and also Explain. [7M]
- 3 a) Explain the construction and working of Photo diode. [7M]  
b) Explain construction and operation of full wave rectifier with L section filter? [7M]  
Or
- 4 a) Explain construction and operation of a bridge rectifier and find PIV, RMS current, Rectifier efficiency & Ripple factor. [7M]  
b) Discuss how full wave rectification differs from half wave rectification. [7M]
- 5 a) With neat sketch explain the operation & Drain, Gate characteristics of Depletion MOSFET. [7M]  
b) Explain about punch through effect? [7M]  
Or
- 6 a) Explain how the transistor acts as an amplifier? [7M]  
b) Compare & contrast BJT & FET. [7M]
- 7 a) Explain the need for biasing in electronic circuits. What are the factors affecting the stability factor. [7M]  
b) Derive the equation for stability factor for fixed bias. [7M]  
Or
- 8 a) Determine the quiescent currents and the collector to emitter voltage for a Ge transistor with  $\beta = 50$  in the self-biasing arrangements. The circuit component values are  $V_{CC} = 20V$ ,  $R_C = 2k\Omega$ ,  $R_e = 0.1 k\Omega$ ,  $R_1 = 100 k\Omega$  and  $R_2 = 5 k\Omega$ . Find the stability factor S. [7M]  
b) Explain in detail about Thermal Runaway & Thermal Stability concepts. [7M]
- 9 Derive the expressions for voltage gain, current gain, input impedance, output impedance, with respect to source and current gain W.r.to source for generalized transistor amplifier at low frequencies. [14M]  
Or
- 10 a) Give the comparison of CE, CB and CC amplifiers with respect to voltage gain, current gain, input impedance and output impedance. [7M]  
b) Compare CS, CD JFET amplifiers. [7M]

