

**II B. Tech I Semester Regular/Supplementary Examinations, January-2023**  
**ELECTRONIC DEVICES AND CIRCUITS**  
 (Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions, each Question from each unit  
 All Questions carry **Equal** Marks

~~~~~  
 UNIT-I

- 1 a) Derive an expression for continuity equation and explain its importance. [7M]  
 b) Define Fermi level and explain its significance in the energy band diagrams. [7M]

OR

- 2 a) Draw and explain the V-I characteristics of PN junction diode. [7M]  
 b) The reverse bias saturation current for a P-N junction diode (Silicon type) is  $2\mu\text{A}$  at 300K. Calculate the dynamic and static resistances at 100mV forward bias at 300K. [7M]

UNIT-II

- 3 a) Draw the symbol of Tunnel diode. Explain the construction and tunneling phenomenon of Tunnel diode. [10M]  
 b) Explain how zener diode acts as a voltage regulator. [4M]

OR

- 4 a) With the help of neat circuit diagram, explain the operation of Bridge rectifier. [8M]  
 b) Compare the performance of inductive, L-section and  $\pi$ -section filters. [4M]  
 c) What is peak inverse voltage (PIV) of a diode in a rectifier circuit? [2M]

UNIT-III

- 5 a) Define  $\alpha$ ,  $\beta$  and  $\gamma$  of a transistor. Show how they are related to each other. [4M]  
 b) Explain about transistor as an amplifier. [5M]  
 c) Explain the operation of photo transistor. [5M]

OR

- 6 a) Explain the working of a depletion-type MOSFET. [7M]  
 b) For n-Channel JFET,  $V_{DS}=10\text{V}$  and  $V_{GS}$  is changed from 3V to 4V and drain current changed  $-4\text{mA}$  to  $2\text{nA}$ . Find  $g_m$ ,  $r_d$ , and  $\mu$  if  $V_{DS}$  changes from 8 to 12V and  $I_D$  changes from 3 to 3.2mA at  $V_{GS}=2.5\text{V}$ . [7M]



## UNIT-IV

- 7 a) Explain about the need for biasing in electronic circuits. What are the factors affecting the stability factor? [6M]
- b) A silicon transistor with  $\beta=70$  is used in self biasing arrangement with  $V_{CC} = 15V$ ,  $R_C = 4.7K\Omega$ . The operating point Q is at  $V_{CE} = 8.2V$ ,  $I_C = 1.2mA$ . Find the values of  $R_1$  and  $R_2$ . [6M]
- c) Define stability factor 'S'. [2M]

## OR

- 8 a) Explain how the Q-point is obtained graphically. [5M]
- b) Explain diode compensation against variation in base-emitter voltage  $V_{BE}$ . [6M]
- c) In a silicon transistor circuit with a fixed bias,  $V_{CC} = 10V$ ,  $R_C = 3K\Omega$ ,  $R_B = 6K\Omega$ ,  $\beta = 100$ ,  $V_{BE} = 0.7V$ . Find the stability factor. [3M]

## UNIT-V

- 9 a) What are the benefits of h-parameters? [2M]
- b) Draw the h-parameter equivalent circuit for a typical common base amplifier and derive expressions for  $A_i$  and  $A_v$ . [8M]
- c) Define the three small-signal parameters of the FET. How are they inter-related? [4M]

## OR

- 10 a) Give the complete analysis of CE transistor amplifier circuit using h-parameters and derive the expressions for current gain, voltage gain, input impedance and output admittance. [12M]
- b) Draw the small signal model of FET. [2M]



**II B. Tech I Semester Regular/Supplementary Examinations, January-2023**  
**ELECTRONIC DEVICES AND CIRCUITS**  
 (Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions, each Question from each unit  
 All Questions carry **Equal** Marks

~~~~~

UNIT-I

- 1 a) Explain about Hall effect. [5M]  
 b) The Hall-coefficient of specimen doped silicon is found to be  $3.66 \times 10^{-4} \text{ m}^3\text{C}$ ; the resistivity of the specimen is  $8.93 \times 10^{-3} \Omega\text{-m}$ . Find the mobility and density of charge carriers assuming single carriers conduction. [4M]  
 c) Explain about Law of junction. [5M]

OR

- 2 a) Briefly explain about Open circuited p-n junction and Biased p-n junction. [10M]  
 b) A silicon diode has a saturation current of  $6.5 \mu\text{A}$  at room temperature 300K. Calculate the saturation current at 400K. [4M]

UNIT-II

- 3 a) Explain the construction and operation of SCR. [8M]  
 b) Draw and explain the V-I characteristics of Varactor diode. [6M]

OR

- 4 a) With a neat sketch explain the operation of center tapped full wave rectifier and derive the expression for ripple factor. [9M]  
 b) Determine the ripple factors of an L-section filter and Capacitive filter with  $C=40\mu\text{F}$ ,  $V_{dc}=12\text{V}$ ,  $R_L=10 \text{ K}\Omega$ ,  $f=50\text{Hz}$  and  $L=10\text{H}$  used with FWR. [5M]

UNIT-III

- 5 a) Explain the various current components in BJT. [7M]  
 b) Draw the Ebers-Moll model of a transistor for NPN transistor and explain the same. [7M]

OR

- 6 a) Define the following terms for a JFET: [7M]  
 (i) The pinch-off voltage  
 (ii)  $I_{DSS}$   
 (iii)  $I_{GSS}$   
 (iv) Drain resistance  
 b) Explain the working of an enhancement-type MOSFET. [7M]



## UNIT-IV

- 7 a) Draw the Fixed bias circuit and derive the expression for the stability factor S. [8M]  
What are the limitations of this circuit?  
b) What is thermal runaway in transistors? Obtain the condition for thermal stability in transistors. [6M]

OR

- 8 a) Explain why bias stabilization is needed in a transistor amplifier circuit. [6M]  
b) In a self biased circuit, the Q-point is established at  $V_{CE} = 12V$  and  $I_C = 2mA$ . Determine  $R_E$ ,  $R_1$  and  $R_2$  so that  $S(I_{C0}) = 3$ . Assume  $\beta = 50$ ,  $V_{BE} = 0.7V$ ,  $V_{CC} = 22.5V$  [8M]

## UNIT-V

- 9 a) Draw the small signal model of FET and explain the significance of each element. [5M]  
b) A CE amplifier is drawn by a voltage source of internal resistance  $r_s = 700 \Omega$ , and the load impedance is a resistance  $R_L = 1000\Omega$ . The h-parameters are  $h_{ie} = 1K\Omega$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{fe} = 50$  and  $h_{oe} = 25 \mu A/V$ . Compute the current gain, input resistance, voltage gain and output resistance. [9M]

OR

- 10 a) Derive the expressions for voltage gain, current gain, input and output impedance of CC amplifier using exact and approximate analysis. [10M]  
b) Give the comparison of transistor amplifiers. [4M]



**II B. Tech I Semester Regular/Supplementary Examinations, January-2023**  
**ELECTRONIC DEVICES AND CIRCUITS**  
 (Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions, each Question from each unit  
 All Questions carry **Equal** Marks

UNIT-I

- 1 a) Explain energy band diagrams of intrinsic and extrinsic semiconductors with neat sketches. [7M]  
 b) Derive an expression for the Fermi level in an intrinsic semiconductor. Express electron and hole concentrations in terms of Fermi level. [7M]

OR

- 2 a) Calculate the barrier capacitance of a Germanium p-n junction whose area is 1mm by 1mm and space charge thickness is  $2 \times 10^{-4}$  cm. The dielectric constant of Germanium (relative to free space) is 16. [7M]  
 b) Explain the effect of temperature on characteristics of PN junction diode. [7M]

UNIT-II

- 3 a) In what respect is an LED different from an ordinary PN junction diode? State the applications of LEDs. [6M]  
 b) Discuss the operation of UJT with necessary diagrams. [8M]

OR

- 4 a) With neat sketch explain the operation of full wave rectifier with capacitor filter and derive the expression for ripple factor. [10M]  
 b) In a half-wave rectifier circuit, a voltage of  $12 \sin \omega t$  is applied. The diode has a forward resistance of  $10\Omega$ . The load is  $1.5K\Omega$ . Determine  $I_m$  and  $V_{dc}$ . [4M]

UNIT-III

- 5 a) Explain the operation of transistor in CE configuration and draw its input and output characteristics. [10M]  
 b) A certain transistor has a current gain of 0.99 in CB configuration. Calculate its current gain in the CE configuration and another transistor has  $\beta=70$ , determine its  $\alpha$ . [4M]

OR

- 6 a) Explain how a FET is used as a voltage variable resistor. [5M]  
 b) Give the comparison between JFET and MOSFET. [4M]  
 c) An n-channel JFET has  $I_{DSS} = 10mA$  and  $V_P = -2V$ . Determine the drain source resistance  $r_{DS}$  for (i)  $V_{GS} = 0V$  and (ii)  $V_{GS} = -0.5V$ . [5M]



## UNIT-IV

- 7 a) Explain the importance of biasing. [4M]  
b) Define the three stability factors. [3M]  
c) Design a self-bias circuit using silicon transistor to achieve a stability factor of 10, with the following specifications:  $V_{CC}=15V$ ,  $V_{BE}=0.7V$ ,  $V_{CEQ}=8V$ ,  $I_{CQ}=4\text{ mA}$  and  $\beta=50$ . [7M]

OR

- 8 a) Explain why the self-biasing arrangement cannot be used in an enhancement type MOSFET. [4M]  
b) With a neat sketch, explain the operation of collector to base bias. [6M]  
c) Explain how thermistor is used for bias compensation. [4M]

## UNIT-V

- 9 Derive the expressions for voltage gain, current gain, input impedance and output impedance of CE amplifier using exact and approximate analysis. [14M]

OR

- 10 a) Define the various h-parameters and give their units. [3M]  
b) Draw the h-parameter model for common collector configuration. [2M]  
c) Deduce the expressions for input impedance, output impedance and voltage gain of Common Drain amplifier. [9M]



**II B. Tech I Semester Regular/Supplementary Examinations, January-2023**  
**ELECTRONIC DEVICES AND CIRCUITS**  
 (Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions, each Question from each unit  
 All Questions carry **Equal** Marks

~~~~~  
 UNIT-I

- 1 a) What is meant by Fermi level in semiconductor? Where does the Fermi level lie in an intrinsic semiconductor? Prove that the Fermi level in an n-type material is much closer to the conduction band. [7M]  
 b) Explain about Fermi-Dirac function. [7M]

OR

- 2 a) "The barrier potential developed across an open-circuited PN junction allows the flow of minority carriers". Explain how the current due to this flow of charge carriers is counterbalanced. [7M]  
 b) Explain about the current components in PN junction diode. [7M]

UNIT-II

- 3 a) Draw and explain the V-I characteristics of Photodiode. [6M]  
 b) A 10V zener diode is used to regulate the voltage across the variable load  $R_L$ .  $V_{DC}$  has the range  $13V \leq V_{DC} \leq 16V$  and load current is  $10 mA \leq I_L \leq 85 mA$ . Given  $I_{zmin}$  as 15mA, calculate: (i)  $R_S$  and (ii) zener diode power dissipation  $P_Z$ . [8M]

OR

- 4 a) Sketch the circuit of a half-rectifier and explain its operation. [6M]  
 b) A sinusoidal voltage whose  $V_m = 25V$  is applied to a half-wave rectifier. The diode may be considered to be ideal and  $R_L = 1.5 K\Omega$  is connected as load. Determine the following: [6M]  
     (i) Peak value of current  
     (ii) RMS value of current  
     (iii) Ripple factor  
 c) Define form factor. [2M]

UNIT-III

- 5 a) Draw and explain the input and output characteristics of BJT in common base configuration. [8M]  
 b) Explain about punch through/reach through in BJT. [6M]

OR

- 6 Explain the construction and operation of n-channel JFET with neat sketches. Discuss its drain and transfer characteristics. [14M]



## UNIT-IV

- 7 a) Explain why it is considered better to fix the quiescent operating point in the middle of the active region. [4M]  
b) Give the comparisons among fixed, collector to base and self-bias circuits. [3M]  
c) Explain about the transistorized bias compensation against the variation in base-emitter voltage  $V_{BE}$ . [7M]

OR

- 8 a) What are the limitations in selecting the operating region in a transistor circuit? [3M]  
b) Draw the various biasing circuits used for JFET/MOSFET. [6M]  
c) An N-channel JFET with  $V_P = 2.0V$  and  $I_{DSS} = 1.75mA$  is used in an amplifier, using self-bias circuit. It uses a drain-source supply  $V_{DD} = 25V$ . It is desired to bias the circuit at  $I_D=1mA$ . Find (i)  $V_{GS}$  and (ii)  $R_S$ . [5M]

## UNIT-V

- 9 a) Determine the current gain and input impedance when the transistor is connected in CB configuration with a load  $R_L=10K\Omega$ ,  $V_{CB}=10V$ ,  $I_C=1.5mA$ ,  $h_{ib}=20\Omega$ ,  $h_{rb}=5 \times 10^{-4}$ ,  $h_{fb} = -0.98$ ,  $h_{ob}=10^{-7} \Omega^{-1}$ . [6M]  
b) Deduce the expressions for input impedance, output impedance and voltage gain of Common Source amplifier. [8M]

OR

- 10 a) Explain in detail about the small signal analysis of Common Source FET amplifier. [10M]  
b) Discuss the generalized analysis of transistor amplifier model using h-arameters. [4M]

