

II B. Tech I Semester Regular/Supplementary Examinations, December-2023
SWITCHING THEORY AND LOGIC DESIGN
 (Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unit
 All Questions carry **Equal** Marks

UNIT-I

- 1 a) Convert the number $(127.75)_8$ to base 10, base 3, base 16 and base 2. [7M]
 b) Perform subtraction on the following unsigned binary numbers using the 2's complement of the subtrahend (a) $(11011)_2 - (11001)_2$ (b) $(110100)_2 - (10101)_2$ [7M]

OR

- 2 a) Given the 4 bit data word 1011, generate the hamming code that corrects and detects single errors and also explain the error correction capability. [7M]
 b) Express the function $Y = A + B'C$ in canonical SOP and canonical POS form. [7M]

UNIT-II

- 3 a) Simplify the following function using K-map. $F(A,B,C,D) = \Sigma(1,3,4,5,6,11,13,14,15)$ [7M]
 b) Assess a full adder using two half adders and an OR gate. [7M]

OR

- 4 a) Design a code converter for BCD to gray code conversion [7M]
 b) For the given function $T(w,x,y,z) = \Sigma(0,1,5,7,8,10,14,15)$ [7M]
 i) Show on the map ii) Find all prime implicants and indicate which are essential. iii) Find a minimal expression

UNIT-III

- 5 a) Design a priority encoder using logic gates. [7M]
 b) Implement the following functions using PLA with three inputs, four product terms and two outputs. $F1(A, B, C) = \Sigma m(3, 5, 6, 7)$, $F2(A, B, C) = \Sigma m(0, 2, 4, 7)$. [7M]

OR

- 6 a) Implement $F = \Sigma(0,1,2,3)$ using decoder, [7M]
 b) Draw the pin diagrams of Ics 7442 and 7447. Explain their functions. [7M]

UNIT-IV

- 7 a) Draw the state diagram and characteristic table of Master Slave JK flip-flop. [7M]
 b) Design a 3 bit synchronous up counter using T Flip-flops [7M]

OR



- 8 a) Design and explain the working of a synchronous MOD-5 counter. [7M]
 b) Explain the term Race around condition. How is it satisfied by Master-slave Flip-Flops. [7M]

UNIT-V

- 9 a) Convert the following Mealy machine into a corresponding Moore machine: [10M]

Present State	Next State			
	a		b	
	State	O/P	State	O/P
q ₁	q ₁	1	q ₂	0
q ₂	q ₄	1	q ₄	1
q ₃	q ₂	1	q ₃	1
q ₄	q ₃	0	q ₁	1

- b) What is FSM state? List its two basic types. [4M]

OR

- 10 a) What is meant by state diagram? Define how state assignment is important in a sequential circuit design. Describe with a suitable example. [7M]
 b) Design a FSM which detects 0011 pattern and set $z = 1$ for all other patterns $z = 0$. [7M]



II B. Tech I Semester Regular/Supplementary Examinations, December-2023
SWITCHING THEORY AND LOGIC DESIGN
 (Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unit
 All Questions carry **Equal** Marks

~~~~~  
 UNIT-I

- 1 a) Assess the following Excess-3 numbers into decimal numbers. [7M]  
 (i)  $(1011)_2$  (ii)  $(1001\ 0011\ 0111)_2$   
 b) Simplify the following: i)  $(A + AC + B)$  ii)  $F = AB(C + C) + AB$  [7M]  
 iii)  $F = (X + Y)(X + Z)$

OR

- 2 a) Given that a frame with bit sequence 1101011011 is transmitted, it has been [7M]  
 received as 1101011010. Examine the method of detecting the error using  
 Hamming code.  
 b) What are the universal gates? Why they are called universal gate? [7M]

UNIT-II

- 3 a) Simplify the Boolean function using K map technique: [7M]  
 $F = \pi M(3, 4, 6, 7, 11, 12, 13, 14, 15)$ .  
 b) Explain a binary adder, which can be used to add two binary numbers? [7M]

OR

- 4 a) Design a Half Subtractor. [7M]  
 b) By using tabulation methods simplify the function: [7M]  
 $Z = f(A, B, C) = A'B'C' + A'B'C + AB'C' + AB'C$

UNIT-III

- 5 a) Design 32:1 Mux using two 16:1 Muxs and one 2:1 Mux. [7M]  
 b) What is PAL? How does it differ from PROM and PLA? [7M]

OR

- 6 a) Draw the logic circuit of a 3 to 8 decoder and explain its working. [7M]  
 b) Draw the logic diagram of 1 to 4 line demultiplexer and discuss on it. [7M]

UNIT-IV

- 7 a) Design a BCD counter using JK Flip-Flops. [7M]  
 b) Analyze SISO and PIPO shift registers with neat logic diagram. [7M]

OR


- 8 a) Implement D and T FFs using JK flip flop. Tabulate the characteristics equation of the three flip flops. [7M]  
 b) Draw the pin diagrams of Ics 7490 and 74121. Explain their functions. [7M]

## UNIT-V

- 9 a) A sequential circuit with two D flip flops A and B, input X and output Y is specified by the following next state and output equations:  $A(t+1) = AX+BX$ ;  $B(t+1) = A'X$ ;  $Y = (A+B)X'$ .  
 (i) Construct the state table.  
 (ii) Draw the state diagram.  
 b) Write the usage of Mealy machine with example. [6M]
 
## OR

- 10 a) For the given state diagram, prepare the state table, state assignment and state reduction tables. [9M]



- b) Examine the state assignment problem. Define its rule. [5M]



**II B. Tech I Semester Regular/Supplementary Examinations, December-2023**  
**SWITCHING THEORY AND LOGIC DESIGN**  
 (Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unit  
 All Questions carry **Equal** Marks

~~~~~  
 UNIT-I

- 1 a) Describe the procedure to get the Hamming code for the binary word 1101100. [7M]
 b) State and Prove the postulates of Boolean Algebra. [7M]

OR

- 2 a) Deduce $FACE_{16}$ in its binary, octal and decimal equivalent. [7M]
 b) Interpret OR gate and AND gate using NAND gates. [7M]

UNIT-II

- 3 a) Simplify the following function using Karnaugh Map. [7M]
 $F(W,X,Y,Z) = \sum m(0,1,3,9,10,12,13,14) + \sum d(2,5,6,11)$
 b) Construct BCD adder and explain the operation. [7M]

OR

- 4 a) Design a 4 bit BCD to Excess-3 code converter [7M]
 b) Use the K-map method to simplify the following 5-variable function [7M]
 $F = \sum(3,6,7,8,10,12,14,17,19,20,21,24,25,27,31)$

UNIT-III

- 5 a) Design a 64:1 MUX using 8:1 MUXs. [7M]
 b) Draw the pin diagrams of IC 7485 and IC 74154. Explain their functions. [7M]

OR

- 6 a) Design a 4 bit comparator circuit using logic gates. [7M]
 b) Implement the following Boolean function using PLA [7M]
 $F_1(w,x,y,z) = \sum(0,1,3,5,9,13)$
 $F_2(w,x,y,z) = \sum(0,2,4,5,7,9,11,15)$

UNIT-IV

- 7 a) Analyze the circuit of a SR flip flop and realize SR flip flop using D flip flop. [7M]
 b) Draw the pin diagrams of IC 7474 and IC 7475. Explain their functions. [7M]


OR



- 8 a) Describe the design procedure with neat diagram about 4 bit bidirectional shift register with parallel load. [7M]
 b) Draw a block diagram of Modulo 10 ripple counter and explain its timing diagram. [7M]

UNIT-V

 - 9 a) Show the state transition diagram of a sequence detector circuit that detects '1010' from input data stream using Moore model. [7M]
 b) A sequential circuit has one input and one output. The state diagram is shown below: [7M]



Design the sequential circuit with D flip-flop

OR

- 10 a) Convert the following Moore machine into a corresponding Mealy machine: [7M]

Present State	Next State		Output
	w=0	w=1	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	E	0

- b) Write the usage of Moore machine with example. [7M]