

II B. Tech I Semester Supplementary Examinations, July - 2022
SWITCHING THEORY AND LOGIC DESIGN
 (Com to ECE, EIE, ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unit
 All Questions carry **Equal** Marks

- ~~~~~
- 1 a) Convert the following (i) $(123.589)_{10} = ()_8$. [7M]
 (ii) $(1011011111101.10101)_2 = ()_{16}$
- b) Represent +35 and -35 in sign magnitude, sign 1's complement and sign 2's complement representation. [4M]
- c) Convert $(525)_{10}$ into its Excess-3 code. [3M]
- Or
- 2 a) Find the complement of the following and show that $F.F'=0$ and $F+F'=1$ [8M]
 (i) $F=XY'+X'Y$
 (ii) $F=(X+Y'+Z)(X'+Z')(X+Y)$
- b) What are universal gates? Why these gates are called as universal gates? [3M]
- c) What are the applications of Boolean algebra? [3M]
- 3 a) Find the minimal sum of products for the Boolean expression, [10M]
 $f = \sum m(1,2,3,5,7,8,9,10,12,14,15)$, using the K-Map.
- b) What is the advantage of tabular method? [2M]
- c) Explain the term prime implicant. [2M]
- Or
- 4 a) Design and implement 4-bit Binary Adder/subtractor. [10M]
- b) What is a full/subtractor? Write its truth table. [2M]
- c) List the applications of full adders. [2M]
- 5 a) With the help of a logic diagram and a truth table, explain a 3-line to 8-line decoder. [7M]
- b) Draw the pin diagram of an IC 7447 and also write its truth table. [4M]
- c) What is multiplexer? List the applications of multiplexers. [3M]
- Or
- 6 a) Design a combinational circuit using PROM that accepts 3-bit binary number and generates its equivalent excess-3 code. [10M]
- b) Briefly explain about PLDs. [4M]


- 7 a) Design a 4-bit synchronous counter with T flip-flops. [10M]
 b) Write a short notes on [4M]
 (i) IC 7490 (ii) IC 74121

Or

- 8 a) Convert SR flip-flop to JK flip-flop with an example. [10M]
 b) Write the differences between combinational and sequential circuits. [4M]
- 9 a) With the help of State table and State diagram explain the operation of Sequence generator. [7M]
 b) With an example explain the procedure for conversion of Moore machine to Mealy machine. [7M]

Or

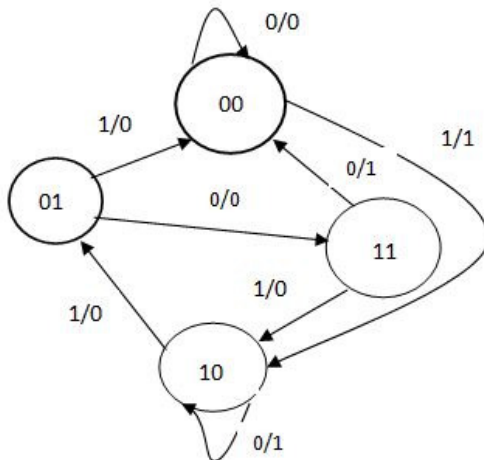- 10 a) A sequential circuit has one input and one output .The state diagram is shown below. Design the sequential circuit with RS flip-flop. [10M]



- b) Distinguish between Moore and Mealy Machines. [4M]

