

II B. Tech II Semester Supplementary Examinations, December- 2023

ELECTRONIC CIRCUIT ANALYSIS

(Common to ECE, EIE, & ECT)

Time: 3 hours

Max. Marks: 70

Answer any FIVE Questions each Question from each unit

All Questions carry Equal Marks

UNIT--I

- 1 a) With relevant mathematical expressions, explain about hybrid- π capacitances. [7M]
 b) Derive the expressions for voltage gain and input admittances of a common drain (CD) amplifier at high frequencies. [7M]

Or

- 2 a) For the following measurements, $I_C = 5 \text{ mA}$, $V_{CE} = 10 \text{ V}$ at room temperature $h_{fe} = 100$, $h_{ie} = 600 \Omega$, $A_{ie} = 10$ at 10 MHz, $C_C = 3 \text{ pF}$. Determine f_{β} , f_T , $r_{b'e}$, $r_{bb'}$ and C_e . [7M]
 b) Derive the expressions for transconductance (g_m) and input conductance ($g_{b'e}$) of a hybrid- π model? Also, mention the typical values of hybrid- π parameters. [7M]

UNIT--II

- 3 a) Derive the overall current gain, voltage gain, input impedance and output impedance of Darlington pair amplifier in terms of h-parameters? [8M]
 b) Three amplifiers of gain 20dB, 30dB and 40dB are connected together. Find the overall gain in dB and normal units. [6M]

Or

- 4 a) List out the advantages, disadvantages and applications of multistage amplifiers. [6M]
 b) Derive the expression for differential mode gain of BJT based differential amplifier. Also, mention the features of differential amplifier. [8M]

UNIT--III

- 5 a) Derive an expression for the voltage gain, input and output impedances with feedback of a voltage series feedback amplifier? [7M]
 b) The mid band gain of an amplifier is 500, the lower cut-off frequency is 70 Hz and upper cut-off frequency is 150 Hz. The mid band gain is reduces to 20 on employing negative feedback. Determine the effect of feedback on the upper and lower cut-off frequency. [7M]

Or

- 6 a) Distinguish between regenerative and degenerative feedback in amplifiers and give their applications. [7M]
 b) Enumerate the procedure employed in the analysis of feedback amplifiers and discuss in detail the effect of feedback on the amplifier parameters. [7M]

UNIT--IV

- 7 a) What is an Oscillator? Explain the Barkhausen criterion for oscillations in sinusoidal oscillator. [7M]
 b) Derive an expression for frequency of oscillations of a Wein bridge oscillator using transistors. Also, mention its advantages. [7M]

Or



- 8 a) In a FET based RC phase shift oscillator, $R = 200 \text{ K}\Omega$ and $C = 200 \text{ pF}$. Find the frequency of the oscillator. [7M]
- b) Derive the expression for frequency of oscillation and conditions of oscillation of a Colpitt's oscillator? Also, mention its applications. [7M]

UNIT--V

- 9 a) A transformer coupled class A power amplifier supplies the power to an $80 \text{ }\Omega$ load connected across the secondary of a transformer having turns ratio of 5:1, if $I_c = 120 \text{ mA}$, determine maximum output power. [7M]
- b) What is class C amplifier? How are harmonics avoided in the output of such an amplifier? [7M]

Or

- 10 a) What is single tuned amplifier? Give its advantages and limitations. [7M]
- b) Draw the equivalent circuit of capacitance coupled single tuned amplifier and derive the expression for voltage gain. [7M]

