

II B. Tech II Semester Regular Examinations, June/July - 2022

ELECTRONIC CIRCUIT ANALYSIS

(Common to ECE, EIE, & ECT)

Time: 3 hours

Max. Marks: 70

Answer any FIVE Questions each Question from each unit
All Questions carry Equal Marks

UNIT-I

- 1 a) Derive the voltage gain equation for common source amplifier at high frequencies. [7M]
b) Explain various high frequency parameters of a BJT and derive the relations between them. [7M]

Or

- 2 Determine the all hybrid $-\pi$ parameters of a Transistor operating at Collector Current $I_C(Q)=2\text{mA}$, $V_{CE}(Q)=20\text{V}$ and $I_B(Q)=20\mu\text{A}$. Transistor specifications are $\beta_0=100$, unity gain frequency $f_T = 50\text{MHz}$, $C_{OB}=3\text{pF}$, $h_{iE}=1.4\text{K}\Omega$, $h_{re}=2.5*10^{-4}$, $h_{oe}=25\mu\text{mhos}$. Assume that the Operating temperature is 300^0K . [14M]

UNIT-II

- 3 a) Draw the circuit of Boot-strap follower and explain its operation. [7M]
b) How Differential amplifier using BJT works?- Discuss. [7M]

Or

- 4 A CE-RC coupled amplifier uses transistor with the following h-parameters: [14M]
 $h_{fe}=50$, $h_{oe}=30*10^{-6}$ mhos, $h_{re}=2.5*10^{-4}$. The value of g_m at the operating point is 50m mhos. The biasing resistor R1 between V_{cc} and base is $100\text{K}\Omega$ and R2 between base and ground is $10\text{K}\Omega$. The load resistor $R_C = 5\text{K}\Omega$. let $C = 160\text{pF}$ be the total shunt capacitance in the input circuit and the coupling capacitor $C_c=6\mu\text{F}$, Calculate for one stage of the amplifier:
(i) mid-band current gain
(ii) mid-band voltage gain

UNIT-III

- 5 a) With neat block diagram, show that input resistance increases with series mixing. [7M]
b) Draw the circuit diagram of a current series feedback amplifier, Derive expressions of input & output impedances, Gain, and feedback factor. [7M]


Or

- 6 a) An amplifier has a gain of 50 with negative feedback. For a specified output voltage, if the input required is 0.1V without feedback and 0.8V with feedback, Compute β and open loop gain. [7M]
b) Explain the concept of feedback with block diagram. What are the merits and demerits of positive feedback? [7M]

UNIT-IV

- 7 a) Derive the expression frequency of oscillation and condition for sustained oscillations of a Colpitts oscillator. [7M]
b) Derive the basic conditions for oscillations and classify oscillators based on their applications. [7M]

Or

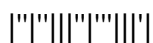

- 8 a) With the help of suitable schematic, explain the operation of a Wien Bridge oscillator and derive an expression for its frequency of operation. [7M]
b) In the Wien-bridge oscillator, if the RC network consists of resistors of $200\text{K}\Omega$ and the capacitors of 300pF , find its frequency of oscillation. [7M]

UNIT-V

- 9 a) Distinguish Single and Double tuned amplifiers. [7M]
b) Derive Q factor of a single tuned amplifier. [7M]

Or

- 10 a) Explain the operation of class A push-pull power amplifier. [7M]
b) Show that the conversion efficiency of a transformer coupled power amplifier is 50%. [7M]



II B. Tech II Semester Regular Examinations, June/July - 2022

ELECTRONIC CIRCUIT ANALYSIS

(Common to ECE, EIE, & ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unitAll Questions carry **Equal** Marks

UNIT-I

- 1 a) Define f_T and derive an expression for it. [7M]
 b) Explain various hybrid-pi capacitances and conductance of a BJT. [7M]

Or

- 2 a) What are the typical values of various components in hybrid $-\pi$ model? Show that at low frequencies the hybrid $-\pi$ model with r_{be} taken as infinite reduces to the approximate CE- h $-\pi$ parameter model. [7M]
 b) A FET has Drain saturation current I_{DSS} of 10mA and Quiescent point Drain current I_D is 5mA, with pinch-off voltage $V_p = -4V$, calculate the value of V_{GS} and the value of Trans conductance gm. [7M]

UNIT-II

- 3 a) Derive an expression for the overall higher cut-off frequency of a two stage amplifier with identical stages of individual higher cut-off frequency, f_H . [7M]
 b) Discuss about the effect of cascading on bandwidth of multistage amplifiers. [7M]

Or

- 4 a) Discuss the effect of coupling capacitors of a CE amplifier on the over all frequency response of the amplifier. [7M]
 b) Draw the circuit diagram, equivalent circuit of a Darlington pair and derive expressions for overall voltage gain and input impedance. [7M]

UNIT-III

- 5 a) Explain the concept of feedback with block diagrams? What are the advantages and disadvantages of negative feedback? [7M]
 b) An amplifier has a gain of 50 with negative feedback. For a specified output voltage, if the input required is 0.1V without feedback and 0.8V with feedback, Compute β and open loop gain. [7M]

Or


- 6 Through the block schematics, [14M]
 i. Explain four types of negative feedback amplifiers.
 ii. Derive and compare their parameters.

UNIT-IV

- 7 a) Derive the expression frequency of oscillation and condition for sustained oscillations of a Colpitt's oscillator. [7M]
 b) Explain the concept of frequency and amplitude stability of oscillators. [7M]


Or

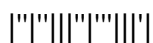- 8 a) Derive the expression frequency of oscillation and condition for sustained oscillations of a FET based RC Phase shift oscillator. [7M]
 b) State and explain Barkhausen criterion with different conditions of Loop gain. [7M]



UNIT-V

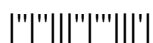- 9 a) Draw the equivalent circuit of capacitance coupled single tuned amplifier and derive the equation for voltage gain. [7M]
b) What is a Q-factor, Derive the expression for Q-factor of a capacitor? [7M]
- Or
- 10 a) Explain the operation of class B Push-Pull power amplifier. [7M]
b) What is a cross over distortion and explain a remedy for it. [7M]



II B. Tech II Semester Regular Examinations, June/July - 2022

ELECTRONIC CIRCUIT ANALYSIS

(Common to ECE, EIE, & ECT)

Time: 3 hours

Max. Marks: 70

Answer any **FIVE** Questions each Question from each unit
All Questions carry **Equal** Marks

~~~~~  
UNIT-I

- 1 a) Perform the high frequency analysis of a common drain amplifier. [7M]  
b) Derive the expression for the high frequency parameters in terms of low Frequency parameters of a BJT. [7M]

Or

- 2 Define Hybrid- $\pi$  model. Draw and derive the expressions for different elements of the Hybrid  $-\pi$  model [14M]  
(i) Determination of Trans Conductance  
(ii) Determination of input conductance  
(iii) Determination of feedback conductance  
(iv) Determination of output conductance

## UNIT-II

- 3 a) With the help of a neat circuit diagram, describe the working of a cascade amplifier. [7M]  
b) Differentiate between direct and capacitive coupling of multiple stages of amplifiers. [7M]  
With the help of a neat circuit diagram, describe the working of a cascade amplifier.

Or

- 4 Draw the equivalent circuits of RC coupled amplifier for Mid-band, Low frequency range, high frequency range and derive the expressions for current gain and voltage gain. [14M]

## UNIT-III

- 5 a) Derive the expression for output resistance of a voltage sampled circuit. [7M]  
b) Explain the method of identifying feedback Topology. [7M]


Or

- 6 a) With a neat sketch explain a negative feedback amplifier and obtain expression for its closed loop gain. [7M]  
b) A voltage-series negative feedback amplifier has a voltage gain without feedback of  $A=500$ , input resistance  $R_i=3K\Omega$ , output resistance of  $R_o=20K\Omega$  and feedback ratio  $\beta=0.01$ , calculate the voltage gain  $A_f$ , input resistance  $R_{if}$  and output resistance  $R_{of}$  of the amplifier with feedback. [7M]

## UNIT-IV

- 7 a) Derive the expression frequency of oscillation and condition for sustained oscillations of a Hartley oscillator. [7M]  
b) In an Hartley oscillator, if  $L_1=0.2mH$ ,  $L_2=0.3mH$  and  $C=0.003 \mu F$ , calculate the frequency of its oscillation. [7M]

Or

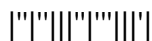


- 8 Discuss and explain the basic circuit of an LC oscillator and derive the condition for the oscillations. [14M]

**UNIT-V**

- 9 a) With the help of a suitable circuit diagram, show that the maximum conversion efficiency of a class B power amplifier is 78.5%. [7M]  
b) Write short notes on Thermal stability and Heat sinks. [7M]

Or

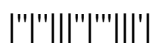- 10 a) Draw the diagram of a capacitance coupled tuned amplifier and derive an expression for its quality factor. [7M]  
b) Define efficiency for a power amplifier. Classify power amplifiers based on their class of operation and compare them. [7M]



## II B. Tech II Semester Regular Examinations, June/July - 2022

## ELECTRONIC CIRCUIT ANALYSIS

(Common to ECE, EIE, &amp; ECT)

Time: 3 hours

Max. Marks: 70

Answer any FIVE Questions each Question from each unit

All Questions carry Equal Marks

~~~~~

UNIT-I

- 1 a) Derive the expression for CE short-circuit current gain with resistive load. [7M]
 b) Derive the expressions for f_T and f_β . [7M]

Or

- 2 Draw the Hybrid- π model for a common emitter transistor. At room temperature (300K) at $I_C=10\text{mA}$ and $V_{CE}=8\text{V}$. $h_{ie}=500$, $h_{oe}=2*10^{-4} \mu\text{s}$, $h_{fe}=100$ and $h_{re}=10^{-4}$. At the same operating point $f_T=50\text{MHz}$ and $c_{ob}=3\text{PF}$. Calculate the values of hybrid- π parameters. [14M]

UNIT-II

- 3 a) Derive the expression for input resistance of a Darlington pair circuit. [7M]
 b) With the help of a neat circuit diagram, describe the working of a bootstrapping. [7M]

Or

- 4 a) Derive expressions for R_i , R_o , A_v & A_i using h-parameter model of a CC- CE amplifier? [7M]
 b) Draw the circuit diagram of Direct Coupled Amplifier and explain its operation in detail. [7M]

UNIT-III

- 5 a) Draw the block diagram of Current Shunt feedback system and derive the expression for R_{if} and R_{of} [7M]
 b) What is meant by negative feedback in amplifier, enumerate the effects of negative feedback on the various characteristics of the amplifier. [7M]


Or

- 6 a) Draw the circuit of a voltage series feedback amplifier and derive the expressions for R_{if} and R_{of} [7M]
 b) With neat block diagram Derive the expression for overall gain of a negative feedback circuit. [7M]

UNIT-IV

- 7 a) Derive the expression for frequency of oscillation of BJT- RC phase-shift oscillator with necessary explanation. [7M]
 b) Discuss about Frequency and amplitude stability of oscillators. [7M]

Or

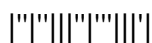

- 8 a) Write down the expression for frequency of oscillation in Hartley and Colpitts Oscillators. [7M]
b) A Colpitts Oscillator is designed with $C_2=100\text{pF}$ and $C_1=7500\text{pF}$. The inductance is variable, determine the range of inductance values, if the frequency of oscillation is to vary between 950 and 2050 KHz. [7M]

UNIT-V

- 9 a) Draw the Class-A Power Amplifier and explain operation in detail with necessary equations. Also derive the expression for maximum conversion efficiency. [7M]
b) What is meant by distortion in power amplifiers, explain the given different types of distortions? [7M]

Or

- 10 a) Explain the reasons for oscillations in a tuned amplifier. Briefly explain the methods used to stabilize the tuned amplifiers against oscillations. [7M]
b) Explain the operation of a double tuned amplifier. Explain the advantages of double tuned circuit over single tuned circuit. [7M]

